

# EWEEK SOLUTIONS

## FEB. 18, 2025 ● SOLUTIONS TO ELECTRICAL ENGINEERING PROBLEM SET

**1.1** In a series circuit, the total resistance is the sum of the individual resistances. Using the given resistances, we have  $150 + 250 + 75 = 475 \Omega$ . So, the total resistance of the circuit is **475  $\Omega$** .

**1.2** In a parallel circuit, the total reciprocal resistance of the system is equal to the sum of the reciprocals of the individual resistances. We have  $1/R_{\text{total}} = 1/150 + 1/250 + 1/75 = 5/750 + 3/750 + 10/750 = 18/750 = 0.024$ . That means  $R_{\text{total}} = 1/0.024 \approx$  **41.67  $\Omega$** .

**1.3** This circuit combines parallel and series configurations. We can start by calculating the resistance of the two  $100 \Omega$  resistors in parallel. We have  $1/R_{\text{parallel}} = 1/100 + 1/100 = 2/100 = 1/50$ , so  $R_{\text{parallel}} = 50 \Omega$ . Next, we can add the parallel combination to the series resistor ( $200 \Omega$ ), giving us  $50 + 200 = 250 \Omega$ . So, the total resistance of this circuit is **250  $\Omega$** .


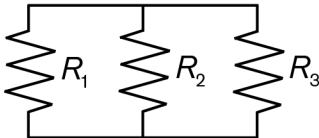
# ELECTRICAL

## TUESDAY, FEBRUARY 18

### EWEEK 2025 ● ELECTRICAL ENGINEERING

**Electrical engineering** powers the technology we rely on every day, from smartphones to advanced medical devices. **Resistors**, a fundamental element in electrical circuits, are crucial for controlling current flow and ensuring circuits function properly, efficiently and safely.

In a **series circuit**, the total resistance is the sum of the individual resistances. In a **parallel circuit**, the total reciprocal resistance of the system is equal to the sum of the reciprocals of the individual resistances. Electrical resistance is measured in **ohms**, represented by the symbol  $\Omega$ .

Series Circuit	Parallel Circuit
 $R_{total} = R_1 + R_2 + R_3 + \dots + R_n$	 $\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$

**1.1** Riya, an electrical engineering student, is designing a prototype for a smartphone charger. To control the flow of current, Riya connects three resistors in series. The first resistor has a resistance of  $150\ \Omega$ , the second has a resistance of  $250\ \Omega$  and the third has a resistance of  $75\ \Omega$ . What is the total resistance of the circuit, in ohms?

**1.2** Riya decides to test a different configuration to see if it will improve the efficiency of the charging circuit. She replaces the series setup with a parallel connection using the same three resistors ( $150\ \Omega$ ,  $250\ \Omega$  and  $75\ \Omega$ ). What is the total resistance of the circuit in this new parallel configuration, in ohms? Express your answer as a decimal to the nearest hundredth.

**1.3** Riya's classmate, Emma, suggests a new design to optimize charging. The design involves two  $100\ \Omega$  resistors connected in parallel, which are then connected in series with a  $200\ \Omega$  resistor. This configuration will power a smartphone charging dock. What is the total resistance of this circuit, in ohms?

